

# EE230: Homework 1

## Familiarization with NGSpice Circuit Simulator

Anubhav Bhatla, 200070008

January 9, 2022

## 1 Overview of the experiment

### 1.1 Aim of the experiment

Familiarization with the basic functions of NGSpice, by creating and simulating the following examples:


- RC Integrator
- RC Differentiator
- RC Lowpass Filter
- RC Highpass Filter
- RC Bandpass Filter
- RLC Bandpass Filter

### 1.2 Methods


The circuit diagrams for the above examples were provided in the lab hand-out, using which I created and simulated them in NGSpice

## 2 Design


### 1. RC Integrator

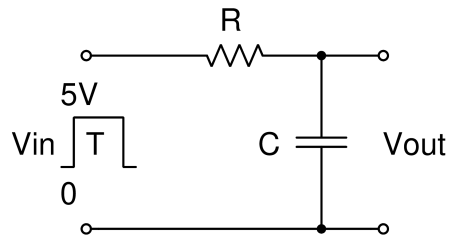


### 2. RC Differentiator

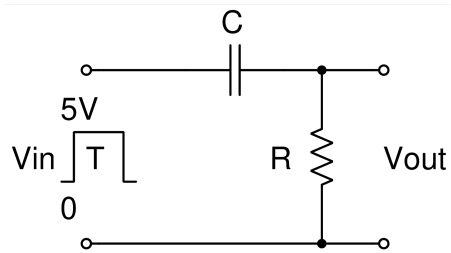


### 3. RC Lowpass Filter

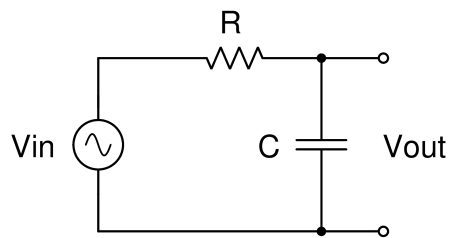


### 4. RC Highpass Filter

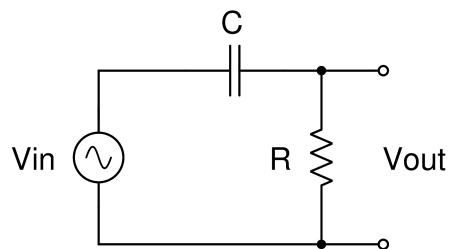

### 5. RC Bandpass Filter

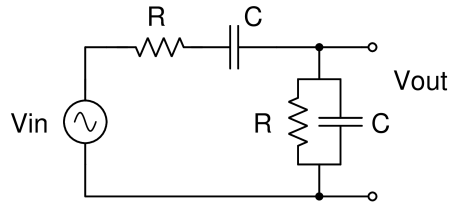

### 6. RLC Bandpass Filter

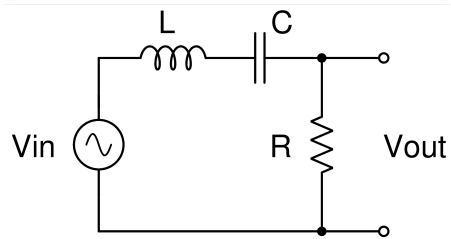

## 3 Simulation results

### 3.1 RC Integrator

#### 3.1.1 Code snippet

```
RC Integrator
*Connections as mentioned in the figure
R 1 2 10k
C 2 0 0.1u
*Input Pulse
Vin 1 0 pulse(0 5 0 0 0 10m 20m)
*Transient Analysis
.tran 0.02m 60m
.control
run
*Plotting Vin and Vout
plot v(1) v(2)
print v(1) v(2)
.endc
```


.end

### 3.1.2 Simulation results


Given below are the plots and reasoning for the 5 cases given for an RC Integrator.

Cases:


1.  $T = 10\tau$

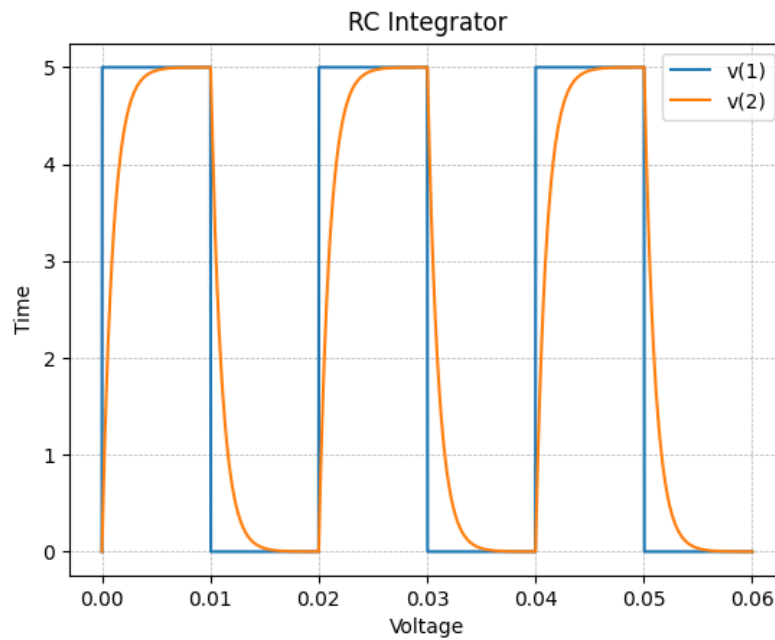


2.  $T = 5\tau$

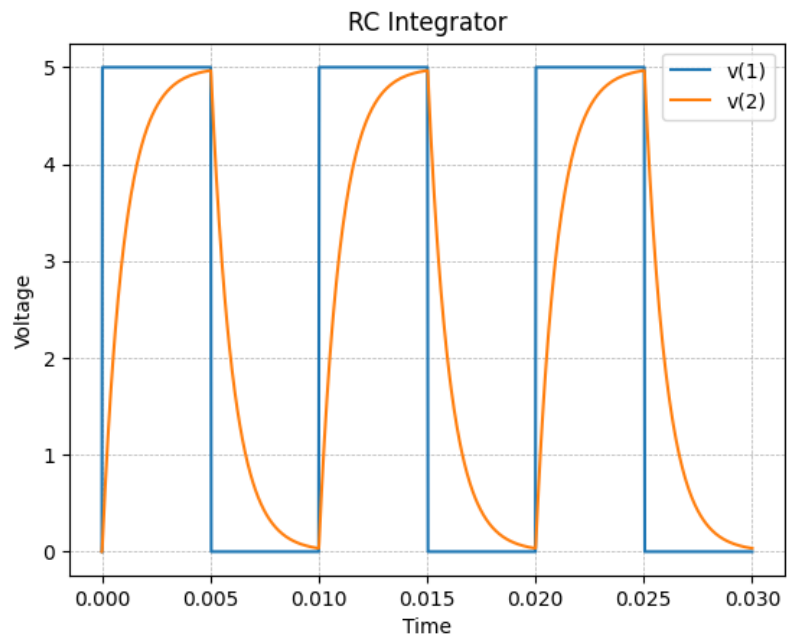


3.  $T = \tau$

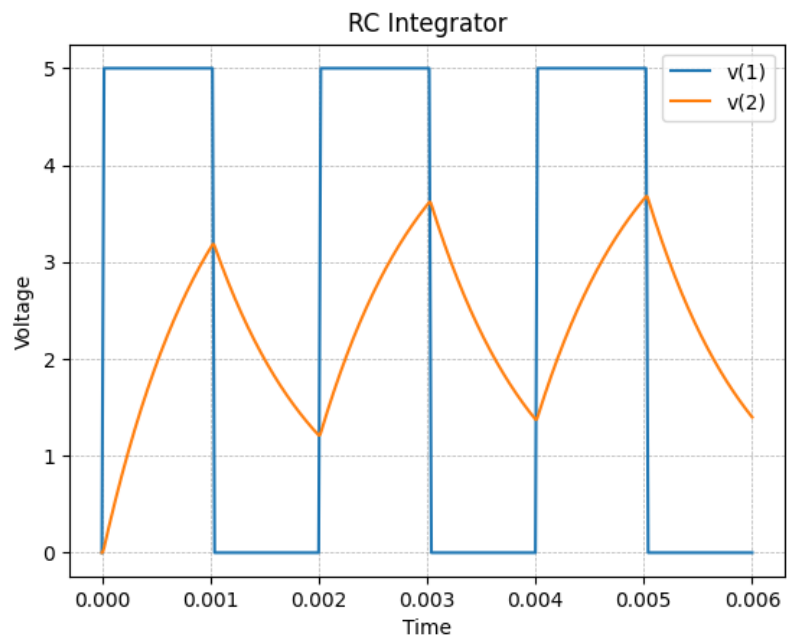

4.  $T = 0.1\tau$

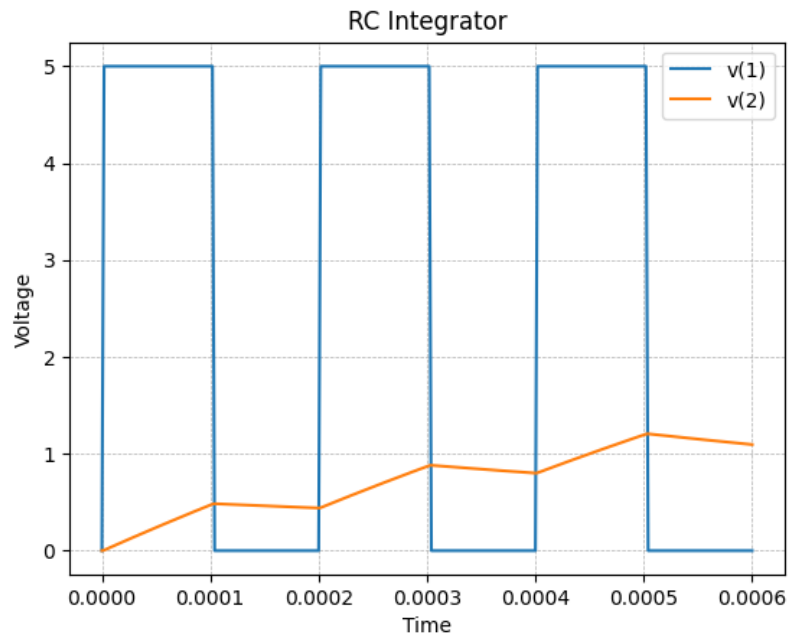

5.  $T = 0.05\tau$

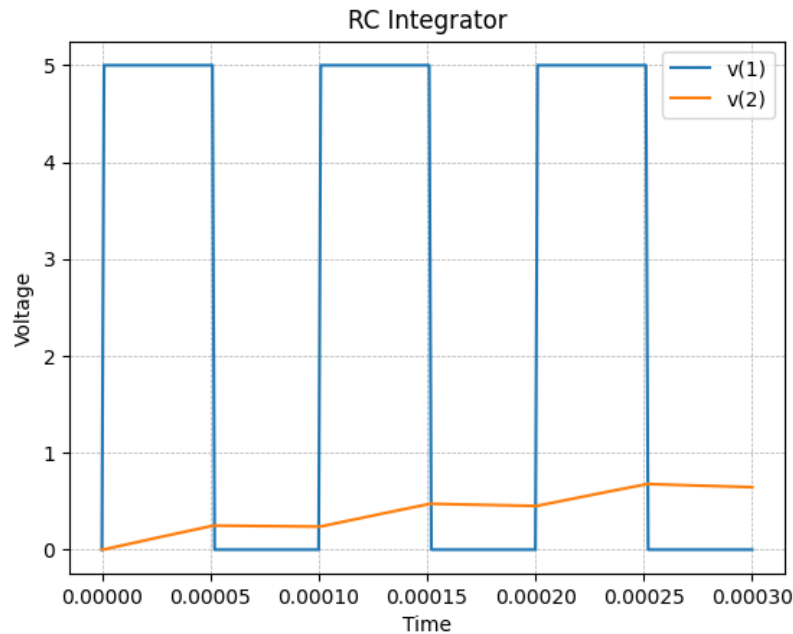

As the Pulse Width to Time Constant ratio decreases, the Capacitor does not get enough time to charge fully and thus we get a lower  $V_{out}$  and a reasonably linear curve. Similarly, for the Discharge cycle, the Capacitor does not get enough time to discharge completely and  $V_{out}$  decreases almost linearly.

## 3.2 RC Differentiator

### 3.2.1 Code snippet

```
RC Differentiator
*Connections as mentioned in the figure
C 1 2 0.1u
R 2 0 10k
*Input Pulse
Vin 1 0 pulse(0 5 0 0 0 10m 20m)
*Transient analysis
.tran 0.02m 60m
.control
run
```

```

*Plotting Vin and Vout
plot v(1) v(2)
print v(1) v(2)
.endc
.end


```

### 3.2.2 Simulation results

Given below are the plots and reasoning for the 5 cases given for an RC Differentiator.


Cases:

1.  $T = 10\tau$

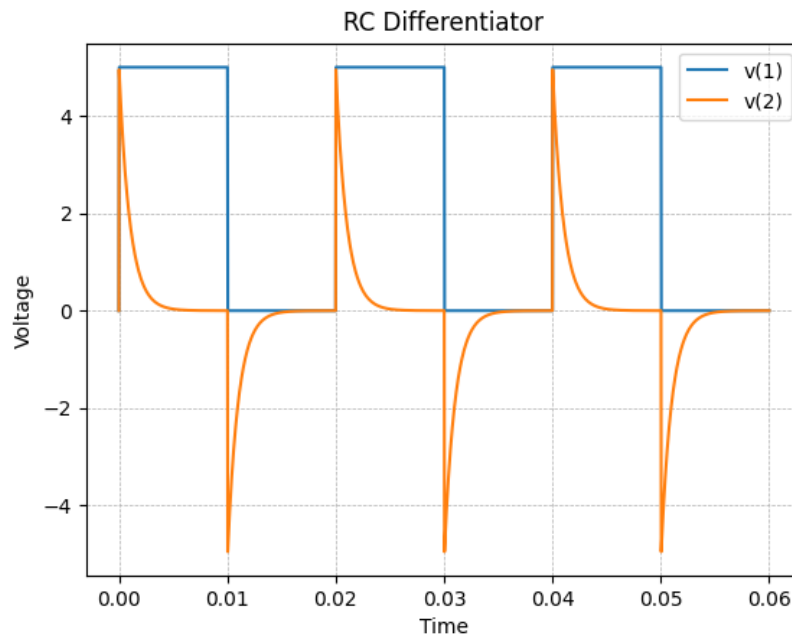


2.  $T = 5\tau$




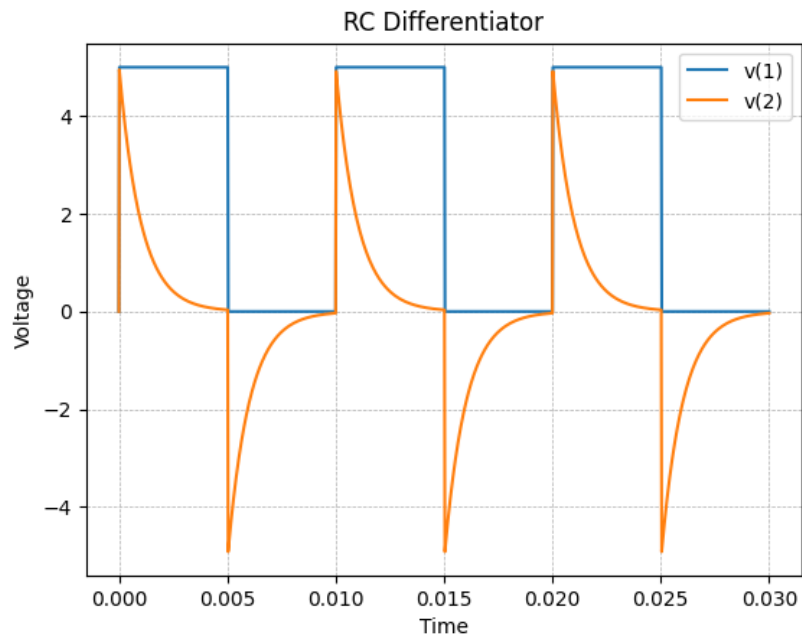


3.  $T = \tau$

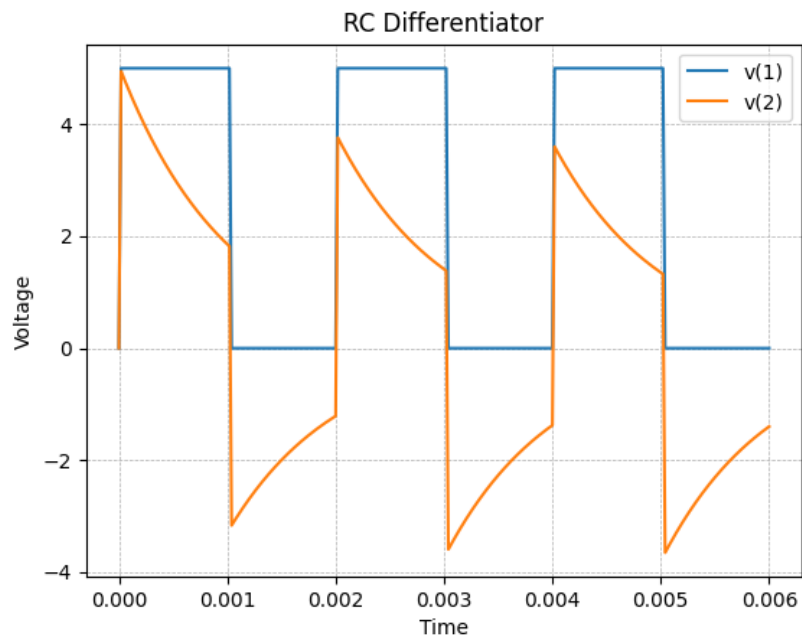

4.  $T = 0.1\tau$

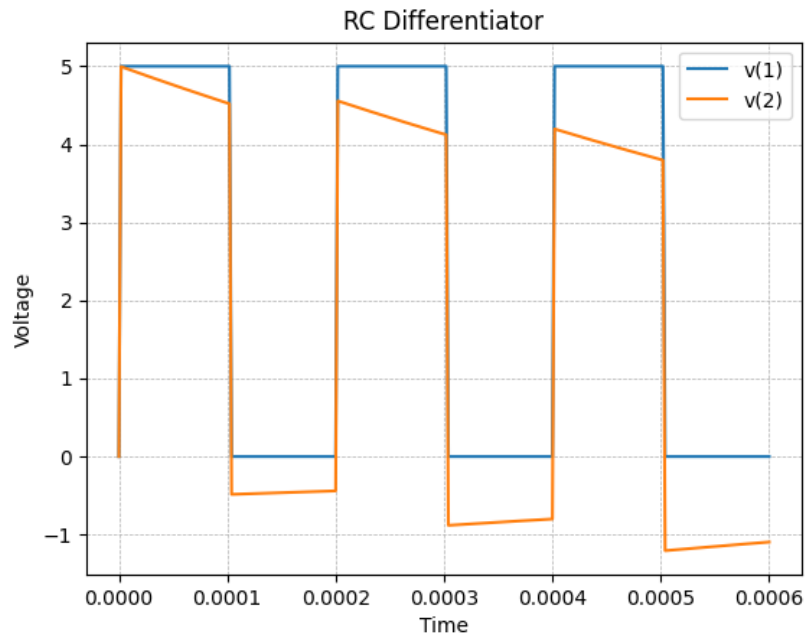

5.  $T = 0.05\tau$

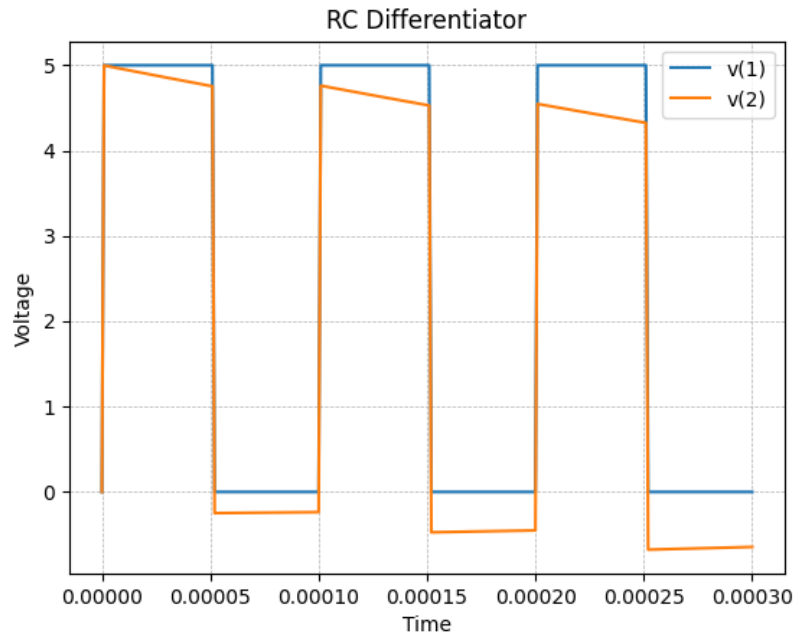

As the Pulse Width to Time Constant ratio decreases, the Capacitor does not get enough time to charge fully and thus we get a large Voltage across the Resistor and a reasonably linear decrease in  $V_{out}$ . Similarly, for the Discharge cycle, the Capacitor does not get enough time to discharge fully and  $V_{out}$  increases almost linearly.

### 3.3 RC Lowpass Filter

#### 3.3.1 Code snippet

RC Lowpass Filter

\*Connections as mentioned in the figure

R 1 2 10k

C 2 0 0.1u

\*AC Input

Vin 1 0 dc 0 ac 1

\*AC analysis

.ac dec 10 1 1Meg

.control


```

run
*Amplitude Bode Plot
plot vdb(2)
print vdb(2)
.endc
.end

```
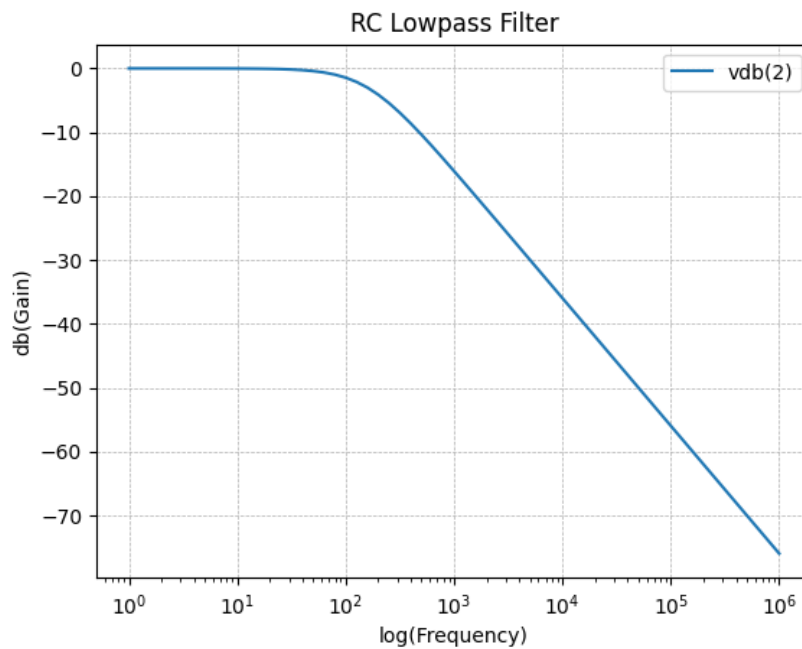
### 3.3.2 Simulation results

Given below is the plot and reasoning for an RC Lowpass Filter.



The filter given above has a 3dB frequency of 158.49 Hz.

## 3.4 RC Highpass Filter

### 3.4.1 Code snippet

```

RC Highpass Filter
*Connections as mentioned in the figure
C 1 2 0.1u
R 2 0 10k

```


```

*AC input
Vin 1 0 dc 0 ac 1
*AC analysis
.ac dec 10 1 1Meg
.control
run
*Amplitude Bode Plot
plot vdb(2)
print vdb(2)
.endc
.end

```
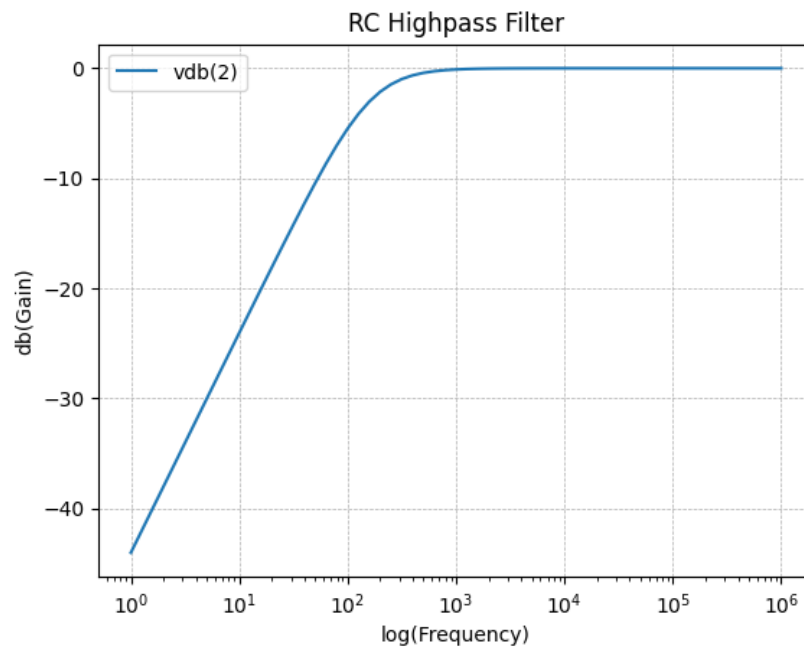
### 3.4.2 Simulation results

Given below is the plot and reasoning for an RC Highpass Filter.



The filter given above has a 3dB frequency of 158.49 Hz.


## 3.5 RC Bandpass Filter

### 3.5.1 Code snippet

```
RC Bandpass Filter
*Connections as mentioned in the figure
R1 1 2 10k
C1 2 3 0.1u
R2 3 0 10k
C2 3 0 0.1u
*AC input
Vin 1 0 dc 0 ac 1
*AC analysis
.ac dec 10 1 1Meg
.control
run
*Amplitude Bode Plot
plot vdb(3)
print vdb(3)
.endc
.end
```
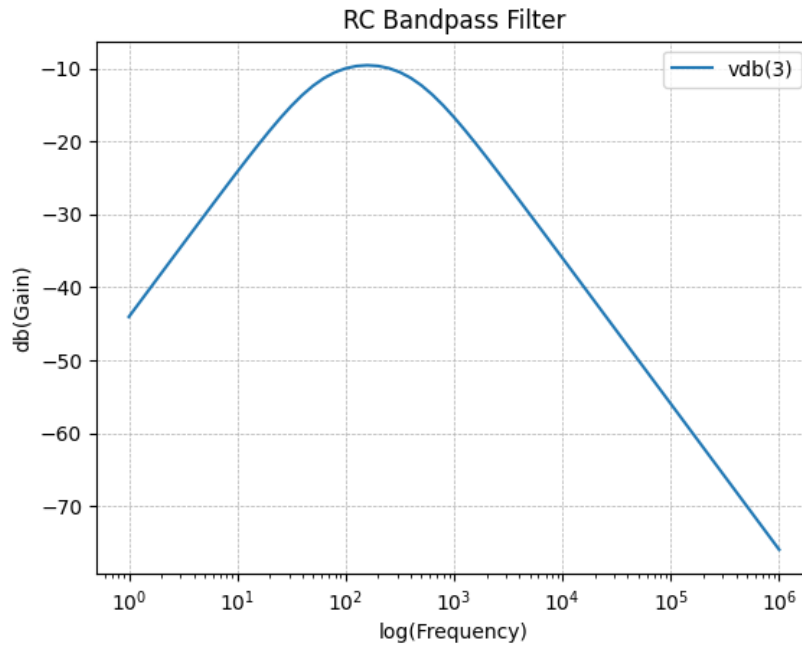
### 3.5.2 Simulation results

Given below is the plot and reasoning for an RC Bandpass Filter.



- **Centre Frequency ( $f_0$ )**  
Theoretical:  $\frac{1}{2\pi RC} = 159.15$  Hz  
Simulation: 158.49 Hz
- **Lower -3dB point ( $f_L$ )**  
Theoretical: 48.31 Hz  
Simulation: 48.306 Hz
- **Higher -3dB point ( $f_H$ )**  
Theoretical: 524.7 Hz  
Simulation: 524.81 Hz

## 3.6 RLC Bandpass Filter

### 3.6.1 Code snippet

RLC Bandpass Filter

\*Connections as mentioned in the figure  
L 1 2 10m


```

C 2 3 0.1u
R 3 0 1k
*AC input
Vin 1 0 dc 0 ac 1
*AC analysis
.ac dec 10 1 1Meg
.control
run
*Amplitude Bode Plot
plot vdb(3)
print vdb(3)
.endc
.end

```
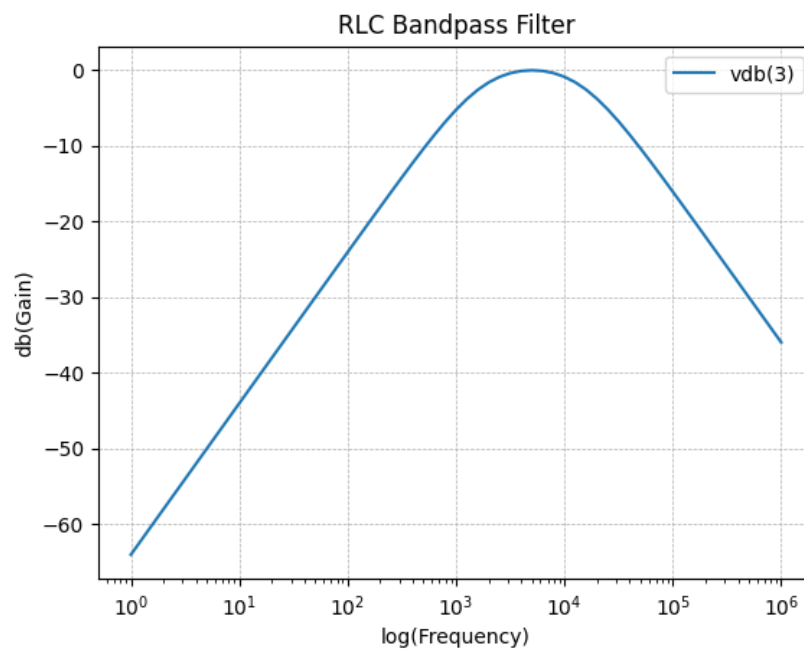
### 3.6.2 Simulation results

Given below is the plot and reasoning for an RLC Bandpass Filter.



- **Centre Frequency ( $f_0$ )**

Theoretical:  $\frac{1}{2\pi\sqrt{LC}} = 5.033 \text{ kHz}$



Simulation: 5.012 kHz

- **Lower -3dB point ( $f_L$ )**

Theoretical:  $\sqrt{\frac{R^2}{2L} + \frac{1}{LC}} - \frac{R}{2L} = 1.458$  kHz

Simulation: 1.445 kHz

- **Higher -3dB point ( $f_H$ )**

Theoretical:  $\sqrt{\frac{R^2}{2L} + \frac{1}{LC}} + \frac{R}{2L} = 17.373$  kHz

Simulation: 17.378 kHz

## 4 Experimental results

### 4.1 RC Integrator

Results of the 5 cases for an RC Integrator are as follows:

Cases:

1.  $T = 10\tau$

Sr. No.	Time	v(1)	v(2)
1	1.196400e-02	0.000000e+00	7.227096e-01
2	2.370065e-02	5.000000e+00	4.875239e+00
3	3.518400e-02	0.000000e+00	2.887281e-02
4	4.776065e-02	5.000000e+00	4.997848e+00
5	5.924400e-02	0.000000e+00	4.979602e-04

2.  $T = 5\tau$

Sr. No.	Time	v(1)	v(2)
1	1.228400e-02	0.000000e+00	3.512221e-03
2	2.369112e-02	5.000000e+00	4.874040e+00
3	3.632400e-02	0.000000e+00	6.179789e-05
4	4.760400e-02	0.000000e+00	3.785714e-01
5	5.920400e-02	0.000000e+00	3.468677e-06

3.  $T = \tau$

Sr. No.	Time	v(1)	v(2)
1	1.228400e-02	0.000000e+00	4.139834e-05
2	2.356400e-02	0.000000e+00	2.536046e-01
3	3.632400e-02	0.000000e+00	7.284082e-07
4	4.760400e-02	0.000000e+00	4.462199e-03
5	5.920400e-02	0.000000e+00	4.088510e-08

4.  $T = 0.1\tau$

Sr. No.	Time	v(1)	v(2)
1	1.228400e-02	0.000000e+00	2.974361e-06
2	2.356400e-02	0.000000e+00	1.822089e-02
3	3.516400e-02	0.000000e+00	1.669497e-07
4	4.760400e-02	0.000000e+00	3.205984e-04
5	5.920400e-02	0.000000e+00	2.937497e-09

5.  $T = 0.05\tau$

Sr. No.	Time	v(1)	v(2)
1	1.227400e-02	0.000000e+00	1.707494e-06
2	2.351400e-02	0.000000e+00	1.088698e-02
3	3.627400e-02	0.000000e+00	3.126979e-08
4	4.751400e-02	0.000000e+00	1.993754e-04
5	5.911400e-02	0.000000e+00	1.826786e-09

## 4.2 RC Differentiator

Results of the 5 cases for an RC Differentiator are as follows:

Cases:

1.  $T = 10\tau$

Sr. No.	Time	v(1)	v(2)
1	1.228400e-02	0.000000e+00	-5.24789e-01
2	2.370065e-02	5.000000e+00	1.247605e-01
3	3.402400e-02	0.000000e+00	-9.21059e-02
4	4.776065e-02	5.000000e+00	2.151705e-03
5	5.924400e-02	0.000000e+00	-4.97960e-04

2.  $T = 5\tau$

Sr. No.	Time	v(1)	v(2)
1	1.228400e-02	0.000000e+00	-3.51222e-03
2	2.369112e-02	5.000000e+00	1.259603e-01
3	3.632400e-02	0.000000e+00	-6.17979e-05
4	4.760400e-02	0.000000e+00	-3.78571e-01
5	5.920400e-02	0.000000e+00	-3.46868e-06

3.  $T = \tau$

Sr. No.	Time	v(1)	v(2)
1	1.228400e-02	0.000000e+00	-4.13983e-05
2	2.356400e-02	0.000000e+00	-2.536046e-01
3	3.632400e-02	0.000000e+00	-7.284082e-07
4	4.760400e-02	0.000000e+00	-4.462199e-03
5	5.920400e-02	0.000000e+00	-4.088510e-08

4.  $T = 0.1\tau$

Sr. No.	Time	v(1)	v(2)
1	1.228400e-02	0.000000e+00	-2.974361e-06
2	2.356400e-02	0.000000e+00	-1.822089e-02
3	3.516400e-02	0.000000e+00	-1.669497e-07
4	4.760400e-02	0.000000e+00	-3.205984e-04
5	5.920400e-02	0.000000e+00	2.937497e-09

5.  $T = 0.05\tau$

Sr. No.	Time	v(1)	v(2)
1	1.227400e-02	0.000000e+00	-1.70749e-06
2	2.351400e-02	0.000000e+00	-1.08870e-02
3	3.627400e-02	0.000000e+00	-9.97524e-08
4	4.751400e-02	0.000000e+00	-1.99375e-04
5	5.911400e-02	0.000000e+00	-1.82679e-09

### 4.3 RC Lowpass Filter

Results of the given RC Lowpass Filter are as follows:

Sr. No.	Frequency	vdb(2)
1	1.584893e+00	-4.30648e-04
2	1.584893e+02	-2.99214e+00
3	1.995262e+03	-2.19911e+01
4	2.511886e+04	-4.39638e+01
5	3.162278e+05	-6.59636e+01

### 4.4 RC Highpass Filter

Results of the given RC Highpass Filter are as follows:

Sr. No.	Frequency	vdb(2)
1	1.258925e+01	-2.20635e+01
2	1.584893e+02	-3.02854e+00
3	1.995262e+03	-2.75452e-02
4	2.511886e+04	-1.74348e-04
5	3.162278e+05	-1.10008e-06

### 4.5 RC Bandpass Filter

Results of the given RC Bandpass Filter are as follows:

Sr. No.	Frequency	vdb(2)
1	1.258925e+01	-2.22227e+01
2	1.584893e+02	-9.54246e+00
3	1.995262e+03	-2.21530e+01
4	2.511886e+04	-4.39648e+01
5	3.162278e+05	-6.59636e+01

### 4.6 RLC Bandpass Filter

Results of the given RLC Bandpass Filter are as follows:

Sr. No.	Frequency	vdb(3)
1	1.258925e+01	-4.20366e+01
2	1.584893e+02	-2.00707e+01
3	1.995262e+03	-1.61962e+00
4	2.511886e+04	-5.17847e+00
5	3.162278e+05	-2.59724e+01