

# EE230: Lab 2

## Zener Regulator & BJT Series Regulator

Anubhav Bhatla, 200070008

January 20, 2022

## 1 Overview of the experiment

### 1.1 Aim of the experiment

1. Creating and Simulating a model of a DC Power Supply with Zener Regulator, finding  $V_{out}$ ,  $I_S$ ,  $I_Z$ ,  $I_L$ , and comparing simulation results with hand calculations.
2. Creating and Simulating a model of a DC Power Supply with BJT Series Regulator, finding the node voltages, and observing  $V_{out}$  with changes in  $R_1$  and  $R_2$ .

### 1.2 Methods

The circuit diagrams for the Zener Regulator and the BJT Series Regulator were provided in the lab handout, using which I created and simulated them in NGSpice.

## 2 Design

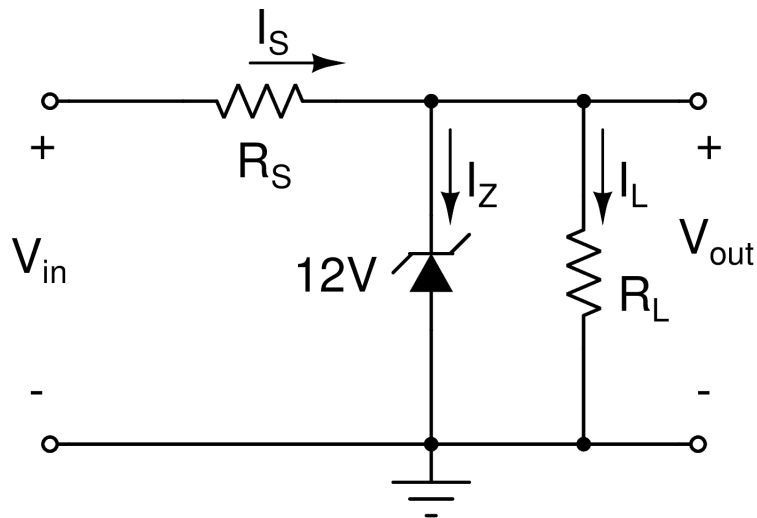


Fig. DC Power Supply with Zener Diode Regulator

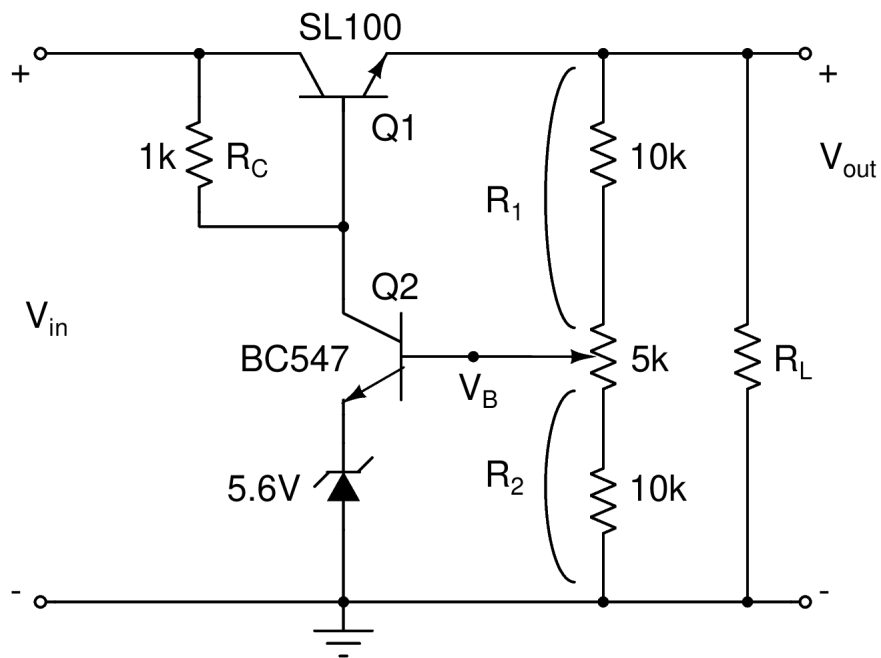


Fig. DC Power Supply with a BJT Series Regulator

## 3 Simulation results


### 3.1 Zener Regulator

#### 3.1.1 Code snippet

```
Zener Regulator
*Zener Subcircuit
.SUBCKT ZENER_12 1 2
D1 1 2 DF
DZ 3 1 DR
VZ 2 3 10.8
.MODEL DF D ( IS=27.5p RS=0.620 N=1.10 CJO=78.3p VJ=1.00
+ M=0.330 TT=50.1n)
.MODEL DR D ( IS=5.49f RS=50 N=1.77 )
.ENDS
Rs 1 dummys 470
Vdummys dummys 2 dc 0
xz dummyz 2 ZENER_12
Vdummyz dummyz 0 dc 0
Rl 2 dummyl 1k
Vdummyl dummyl 0 dc 0
Vin 1 0 dc 20
.op
*.dc Vin 15 25 0.5
.control
run
print v(2) i(Vdummys) i(Vdummyz) i(Vdummyl)
.endc
.end
```

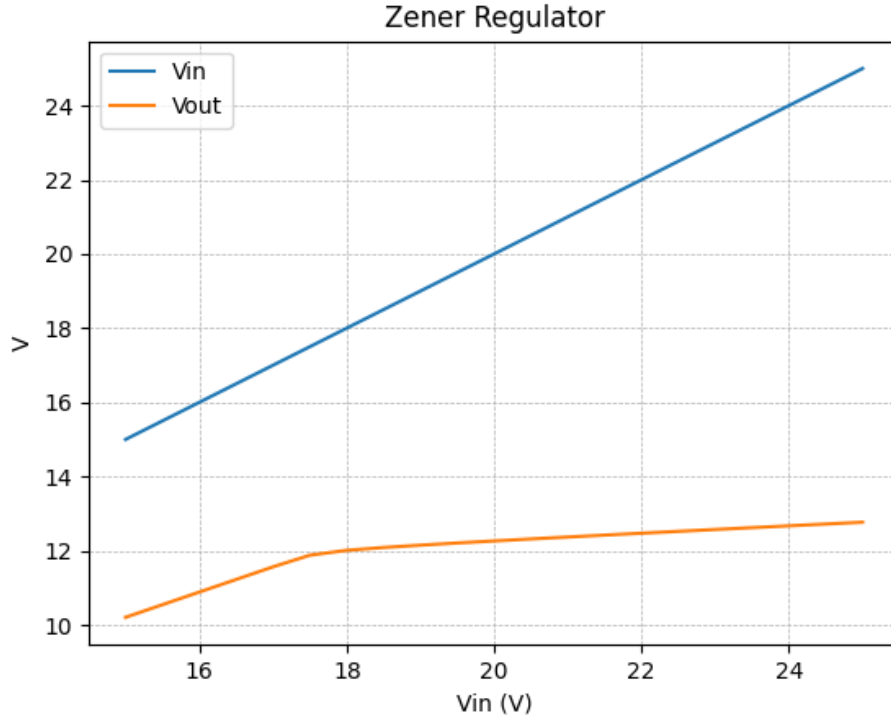
#### 3.1.2 Simulation results

Given below is the plot for  $V_{out}$  waveform obtained from the DC analysis of the Zener Regulator:



We can observe in the graph above that for  $V_{in} > 17.5V$ ,  $V_{out}$  is bound between  $12 - 13V$ . But for  $V_{in} < 17.5V$ , the Zener diode does not regulate the voltage very well around  $12V$ .

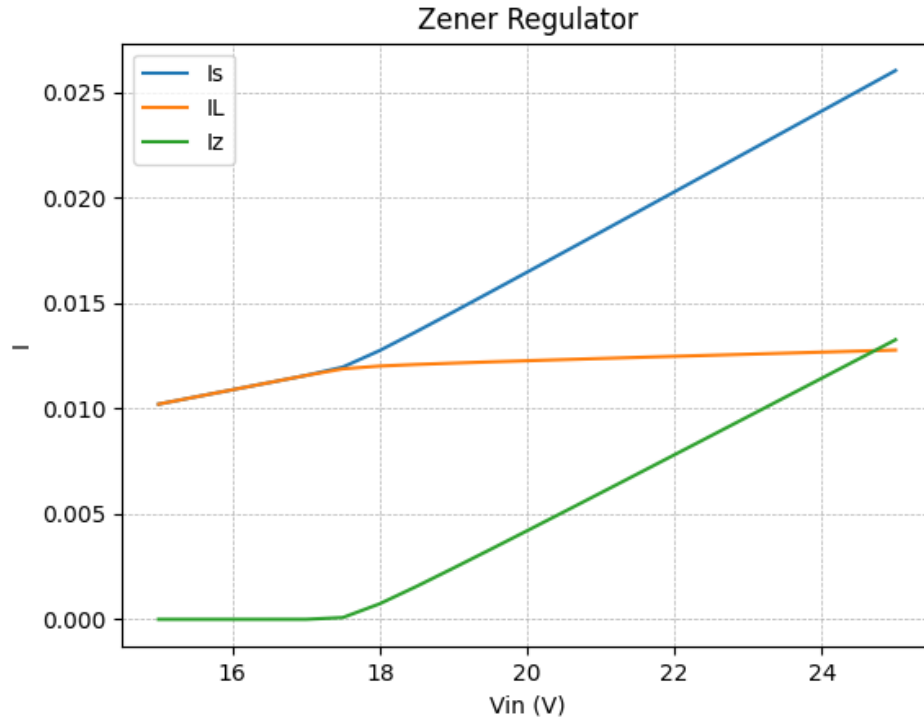Given below is the plot for currents  $I_S$ ,  $I_L$  and  $I_Z$  obtained from the DC analysis of the Zener Regulator:



We can observe in the graph above that for  $V_{in} < 17.5V$ ,  $I_Z$  is approximately 0, which means that the Zener diode is not Reverse Breakdown and thus is not functioning as a Voltage Regulator.

## 3.2 BJT Series Regulator

### 3.2.1 Code snippet

```
BJT Series Regulator
*Zener Subcircuit
.SUBCKT ZENER_12 1 2
D1 1 2 DF
DZ 3 1 DR
VZ 2 3 4.4
.MODEL DF D ( IS=27.5p RS=0.620 N=1.10 CJO=78.3p
+ VJ=1.00 M=0.330 TT=50.1n)
.MODEL DR D ( IS=5.49f RS=50 N=1.77 )
```


```

.ENDS
.model bc547a NPN IS=10f BF=200 ISE=10.3f IKF=50m
+ NE=1.3 BR=9.5 VAF=80 IKR=12m ISC=47p NC=2 VAR=10
+ RB=280 RE=1 RC=40 tr=0.3u tf=0.5n cje=12p vje=0.48
+ mje=0.5 cjc=6p vjc=0.7 mjc=0.33 kf=2f
.model SL100 NPN IS=100f BF=80 ISE=10.3f IKF=50m
+ NE=1.3 BR=9.5 VAF=80 IKR=12m ISC=47p NC=2 VAR=10
+ RB=100 RE=1 RC=10 tr=0.3u tf=0.5n cje=12p vje=0.48
+ mje=0.5 cjc=6p vjc=0.7 mjc=0.33 kf=2f
Rc 1 2 1k
Q1 1 2 3 SL100
Q2 2 4 5 bc547a
xz 0 5 ZENER_12
R1 3 4 10.2k
R2 4 0 14.8k
Rl 3 0 1k
Vin 1 0 dc 20
.op
*.dc Vin 15 25 0.5
.control
run
print v(1) v(2) v(3) v(4) v(5)
.endc
.end

```

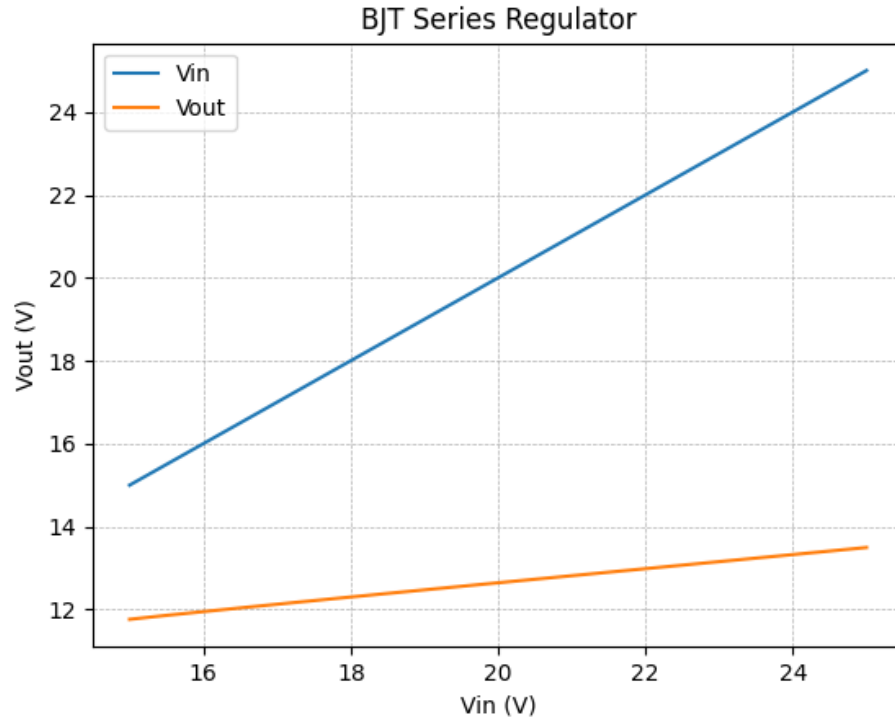
### 3.2.2 Simulation results

Given below is the plot for the  $V_{out}$  waveform obtained from the DC analysis of the BJT Series Regulator:



We can observe that  $V_{out}$  is bound between  $12-14V$  and even for  $V_{in} < 17V$ ,  $V_{out}$  is close to  $12V$ , which means it still regulates unlike the Zener Regulator.

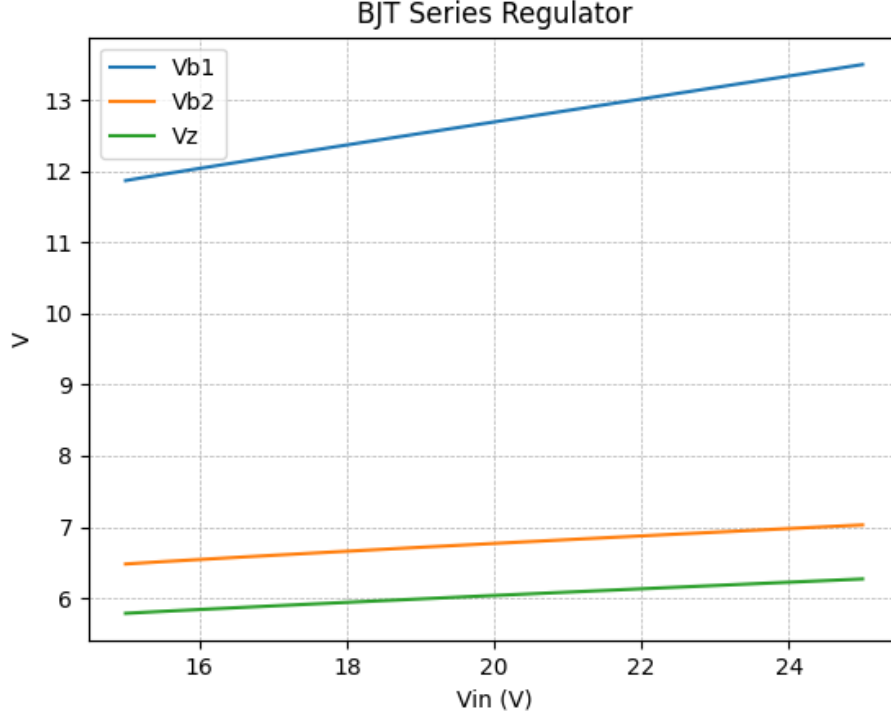Given below is the plot for the node voltages  $V_Z$ ,  $V_{B_1}$  and  $V_{B_2}$  obtained from the DC analysis of the BJT Series Regulator:



## 4 Experimental results

### 4.1 Zener Regulator

Performing Thevenin Analysis for the given Zener Regulator circuit:

$$V_{th} = \frac{V_{in}R_Z + V_ZR_S}{R_S + R_Z} \quad (1)$$

$$R_{th} = R_S || R_Z \quad (2)$$

where  $V_{in}$  is the input voltage applied,  $V_Z = 12V$  is the Zener voltage,  $R_Z = 125\Omega$  is the Zener region diode resistance,  $R_S = 470\Omega$ .

#### 4.1.1 Case (i)

Results of the Voltage and Current readings for the Zener Regulator at  $V_{in} = 20V$  are as follows:



	Theoretical	Simulation
$V_{out}(V)$	1.226269e+01	1.245000e+01
$I_Z(A)$	4.199669e-03	3.600000e-03
$I_S(A)$	1.646236e-02	1.605000e-02
$I_L(A)$	1.226269e-02	1.245000e-02

We can observe that the Theoretical and Simulation readings are reasonably close to each other.

#### 4.1.2 Case (ii)

Results of the Voltage and Current readings obtained from DC analysis of the Zener Regulator are as follows:

Sr. No.	$V_{in}(V)$	$V_{out}(V)$	$I_Z(A)$	$I_S(A)$	$I_L(A)$
1	1.500000e+01	1.020408e+01	3.710268e-11	1.020408e-02	1.020408e-02
2	1.550000e+01	1.054422e+01	3.778295e-11	1.054422e-02	1.054422e-02
3	1.600000e+01	1.088435e+01	3.849787e-11	1.088435e-02	1.088435e-02
4	1.650000e+01	1.122449e+01	9.754691e-11	1.122449e-02	1.122449e-02
5	1.700000e+01	1.156459e+01	9.838411e-08	1.156469e-02	1.156459e-02
6	1.750000e+01	1.187787e+01	8.409802e-05	1.196197e-02	1.187787e-02
7	1.800000e+01	1.200973e+01	7.355326e-04	1.274526e-02	1.200973e-02
8	1.850000e+01	1.208601e+01	1.560762e-03	1.364678e-02	1.208601e-02
9	1.900000e+01	1.214904e+01	2.427471e-03	1.457651e-02	1.214904e-02
10	1.950000e+01	1.220753e+01	3.308364e-03	1.551589e-02	1.220753e-02
11	2.000000e+01	1.226282e+01	4.199255e-03	1.646208e-02	1.226282e-02
12	2.050000e+01	1.231638e+01	5.095567e-03	1.741195e-02	1.231638e-02
13	2.100000e+01	1.236880e+01	5.995462e-03	1.836426e-02	1.236880e-02
14	2.150000e+01	1.242034e+01	6.898083e-03	1.931842e-02	1.242034e-02
15	2.200000e+01	1.247121e+01	7.802798e-03	2.027401e-02	1.247121e-02
16	2.250000e+01	1.252156e+01	8.709161e-03	2.123072e-02	1.252156e-02
17	2.300000e+01	1.257148e+01	9.616852e-03	2.218833e-02	1.257148e-02
18	2.350000e+01	1.262105e+01	1.052564e-02	2.314669e-02	1.262105e-02
19	2.400000e+01	1.267033e+01	1.143534e-02	2.410567e-02	1.267033e-02
20	2.450000e+01	1.271937e+01	1.234582e-02	2.506518e-02	1.271937e-02
21	2.500000e+01	1.276818e+01	1.325696e-02	2.602514e-02	1.276818e-02

For the Zener diode to function properly as a Voltage Regulator, the Voltage across it must be at least  $12V$ . For the limiting case when the Zener diode just stops regulating, we can simply open circuit the Zener and find the voltage across it.

$$V_Z = V_{in} \left( \frac{R_L}{R_S + R_L} \right) \quad (3)$$

For  $V_Z > 12V$ , we get  $V_{in} > 17.64V$

Sr. No.	$V_{in}(V)$	$I_Z(A)$
1	1.500000e+01	3.710268e-11
2	1.550000e+01	3.778295e-11
3	1.600000e+01	3.849787e-11
4	1.650000e+01	9.754691e-11
5	1.700000e+01	9.838411e-08
6	1.750000e+01	8.409802e-05
7	1.800000e+01	7.355326e-04

We can observe that for  $V_{in} < 17.64V$ ,  $I_Z$  is negligible and thus Zener does not act as a Voltage Regulator.

#### 4.1.3 Case (iii)

$$V_Z = V_{in} \left( \frac{R_L}{R_S + R_L} \right) \quad (4)$$

For  $V_Z > 12V$ , we get  $R_L > 705\Omega$

Sr. No.	$R_L(\Omega)$	$V_{out}(V)$
1	500	1.030928e+01
2	600	1.121495e+01
3	705	1.193305e+01
4	800	1.209606e+01
5	900	1.219168e+01

We can observe that for  $R_L < 705\Omega$ ,  $V_{out}$  is not regulated at  $12V$ .

## 4.2 BJT Series Regulator

### 4.2.1 Case (i)

Given below are the Voltage readings at the 5 nodes, obtained using Operational analysis:

$V_{in}(V)$	2.000000e+01
$V_{B_1}(V)$	1.449511e+01
$V_{out}(V)$	1.378716e+01
$V_{B_2}(V)$	6.645576e+00
$V_Z(V)$	5.929149e+00

### 4.2.2 Case (ii)

Given below are the readings for  $V_{out}$  obtained by varying  $R_1$  and  $R_2$ :

Sr. No.	$R_1(k\Omega)$	$R_2(k\Omega)$	$V_{out}(V)$
1	10.2	14.8	1.199875e+01
2	11.5	13.5	1.295299e+01
3	12.5	12.5	1.378716e+01
4	13.5	11.5	1.473014e+01
5	14.5	10.5	1.580584e+01

Using the results obtained above, we get  $R_1 = 10.2k\Omega$  and  $R_2 = 14.8k\Omega$  in order to obtain  $V_{out} = 12V$  at  $V_{in} = 20V$ .

### 4.2.3 Case (iii)

Given below are the readings for  $V_{out}$  obtained separately from Zener and BJT Voltage Regulators:

Sr. No.	$V_{in}$	BJT	Zener
1	1.500000e+01	1.117649e+01	1.020408e+01
2	1.550000e+01	1.126299e+01	1.054422e+01
3	1.600000e+01	1.134652e+01	1.088435e+01
4	1.650000e+01	1.142977e+01	1.122449e+01
5	1.700000e+01	1.151228e+01	1.156459e+01
6	1.750000e+01	1.159418e+01	1.187787e+01
7	1.800000e+01	1.167563e+01	1.200973e+01
8	1.850000e+01	1.175673e+01	1.208601e+01
9	1.900000e+01	1.183757e+01	1.214904e+01
10	1.950000e+01	1.191823e+01	1.220753e+01
11	2.000000e+01	1.199875e+01	1.226282e+01
12	2.050000e+01	1.207920e+01	1.231638e+01
13	2.100000e+01	1.215960e+01	1.236880e+01
14	2.150000e+01	1.224000e+01	1.242034e+01
15	2.200000e+01	1.232042e+01	1.247121e+01
16	2.250000e+01	1.240090e+01	1.252156e+01
17	2.300000e+01	1.248144e+01	1.257148e+01
18	2.350000e+01	1.256207e+01	1.262105e+01
19	2.400000e+01	1.264281e+01	1.267033e+01
20	2.450000e+01	1.272367e+01	1.271937e+01
21	2.500000e+01	1.280466e+01	1.276818e+01

We can observe that the Zener circuit is a better Voltage Regulator than the BJT one as its  $V_{out}$  values are closer to the required 12V. But unlike the Zener circuit, BJT does not require a minimum  $V_{in}$  to function as a Voltage Regulator.